



Subject: Science

Year group: 4

Term: Spring

Unit name: Electricity

Prior Knowledge - Children know about similarities and differences in relation to places, objects, materials and living things. They talk about the features of their own immediate environment and how environments might vary from one another. They make observations of animals and plants and explain why some things occur and talk about changes. (Early Learning Goal)

Scientific enquiry

Classifying	Conductors and insulators Objects which need electricity and those that don't Electrical components When electricity is dangerous
Observing over time	
Pattern seeking	Electrical circuits Bulbs – what makes them brighter/dimmer?
Comparative/fair testing	Electrical circuits
Researching	Alternatives to electricity







National curriculum:

- Identify common appliances that run on electricity.
- Construct a simple series electrical circuit, identifying and naming its basic parts, including cells, wires, bulbs, switches and buzzers.
- Identify whether or not a lamp will light in a simple series circuit, based on whether or not the lamp is part of a complete loop with a battery.
- Recognise that a switch opens and closes a circuit and associate this with whether or not a lamp lights in a simple series circuit.
- Recognise some common conductors and insulators, and associate metals with being good conductors.

Assessment for learning

Recapping prior knowledge- beginning of unit- what do children already know?


Beginning of each lesson- focus on recall of previous learning (quick quizzes)

Topic: Electricity		Year: 4	Strand: Physics
What should I already know? <ul style="list-style-type: none"> • Electricity is a form of energy that can be carried by wires and is used for heating and lighting, and to provide power for devices. • Sources of light and sound may need electricity to work. 		Vocabulary	
What will I know by the end of the unit?			
Where does electricity come from?	<ul style="list-style-type: none"> • Electricity is generated using energy from natural sources such as the Sun, oil, <u>water</u> and wind. • These can also be called fuel sources. 	appliances	a device or machine in your home that you use to do a job such as cleaning or cooking. Appliances are often electrical .
Which appliances run on electricity ?	<ul style="list-style-type: none"> • Some appliances use batteries and some use mains electricity. • Batteries come in different sizes depending on how much and for how long the appliance is used. • Common appliances that use electricity. <div style="display: flex; justify-content: space-around; align-items: center;"> <div style="text-align: center;">  toaster </div> <div style="text-align: center;">  lamp </div> <div style="text-align: center;">  kettle </div> </div> <div style="display: flex; justify-content: space-around; align-items: center; margin-top: 10px;"> <div style="text-align: center;">  laptop </div> <div style="text-align: center;">  X-box </div> <div style="text-align: center;">  phone </div> </div>	battery	small devices that provide the power for electrical items such as torches
		bulb	the glass part of an electric lamp, which gives out light when electricity passes through it.
		buzzer	an electrical device that is used to make a buzzing sound
		cell	a synonym for battery
		circuit	a complete route which an electric current can flow around
		component	the parts that something is made of
		conductor	a substance that <u>heat</u> or electricity can pass through or along
		current	a flow of electricity through a wire or circuit
		device	an object that has been invented for a particular purpose
		electricity	a form of energy that can be carried by wires and in used for heating and lighting, and to provide power for devices
		energy	the power from sources such as electricity that makes machines work or provides heat
		fuel	a substance such as coal, oil, or petrol that is burned to provide heat or power



<p>How does a circuit work?</p>	<ul style="list-style-type: none"> • A complete circuit is a loop that allows electrical current to flow through wires. • A circuit contains a battery (cell), wires and an appliance that requires electricity to work (such as a bulb, motor or buzzer). • The electrical current flows through the wires from the battery (cell) to the bulb, motor or buzzer). • A switch can break or reconnect a circuit. • A switch controls the flow of the electrical current around the circuit. When the switch is off, the current cannot flow. This is not the same as an incomplete circuit.
<p>What are electrical conductors and insulators?</p>	<ul style="list-style-type: none"> • When objects are placed in the circuits, they may or may not allow electricity to pass through. • Objects that are made from materials that allow electricity to pass through a create a complete circuit are called electrical conductors. • Objects that are made from materials that do not allow electricity to pass through and do not complete a circuit are called electrical insulators.

generate	cause it to begin and develop
insulator	a non- conductor of electricity or heat
mains	where the supply of water, electricity , or gas enters a building
motor	a device that uses electricity or fuel to produce movement
power	Power is energy , especially electricity , that is obtained in large quantities from a fuel source and used to operate lights, heating, and machinery
source	where something comes from
switch	a small control for an electrical device which you <u>use</u> to turn the device on or off
wires	a long thin piece of metal that is used to fasten things or to carry electric current

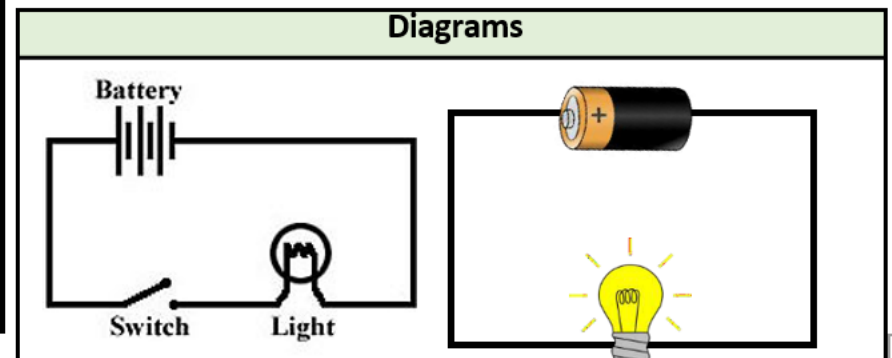


Investigate!

- Research how to work safely with **electricity**.
- Make a variety of **circuits**, investigating which **circuits** work and why.
- Name the basic parts including **cells, batteries, wires, bulbs, switches, motors and buzzers**.
- Draw **circuits** using pictorial representations (not circuit symbols).
- Create **circuits** using **switches**.
- Investigate which materials are **electrical conductors** and **insulators**.

These are complete **circuits** - they have a **battery (cell)** and a **component (bulb)**.

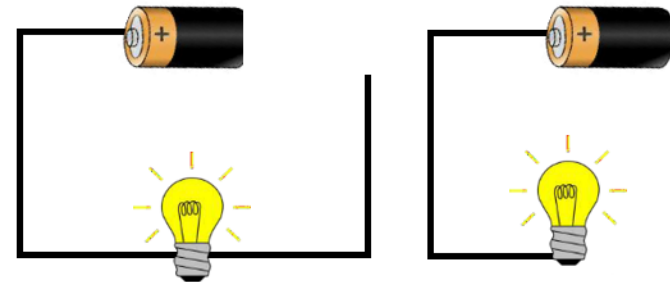The **wires** are placed in the right places of the **battery** for the **circuit** to work.



These **circuits** will not work as they are incomplete.

Lesson Sequence



1. Understand electrical appliances and safety



2. Learn about electrical compounds in a series circuit



3. Investigate electrical circuits



4. Explore conductors and insulators



5. Learn about electrical switches




6. Investigate how electrical components can change within a circuit

Key Facts

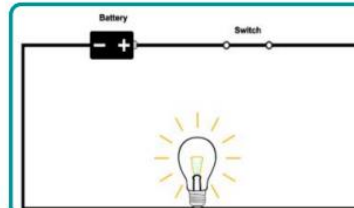1. A circuit contains a battery (cell), wires and a component that requires electricity to work (bulb, motor or buzzer).
2. Electrical current flows through the wires from the battery (cell) to the bulb, motor or buzzer.
3. A switch can break or reconnect a circuit.
4. A switch controls the flow of the electrical current around the circuit. When the switch is off, the current cannot flow. This is not the same as an incomplete circuit.

Conductors and Insulators

- Materials that allow electricity to pass through to create a complete circuit are called electrical conductors.
- Materials that do not allow electricity to pass through and do not complete a circuit are called electrical insulators.




Simple Circuit

A **complete** circuit is a **loop** that allows electrical current to flow through wires.

Simple Electrical Circuit

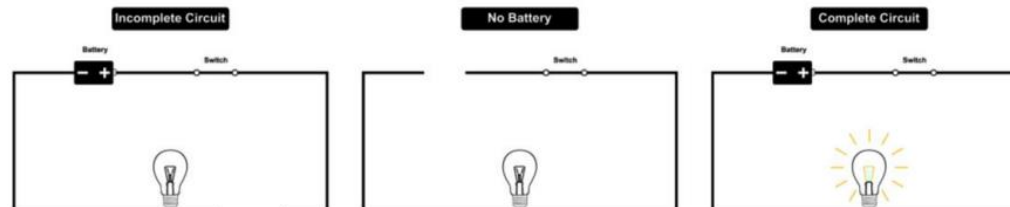These are complete circuits - they have a battery (cell) and a component (bulb). The wires are placed in the right places of the battery for the circuit to work.



These circuits will not work as they are incomplete.

Electrical Components

